

2021 《FPGA 应用实验》实验报告

实验编号： 实验一

实验时间： 2021. 3. 16

实验名称： 利用 8 个发光二极管（LED）形成流水灯显示

班级： F1803603 学号： 518021910534 姓名： 尹俊同

1、实验平台

采用 Xilinx 公司的 FPGA 集成开发环境 Xilinx ISE Design Suite 10.1 sp3，实验开发板为 Xilinx Spartan-3E FPGA Starter Kit。



2、实验设计要求：

在 Spartan-3E FPGA Starter Kit Board 上有 8 个发光二极管（LED7 ~ LED0）。使用开发板的全局时钟信号 CLK_50MHz，管脚为 P=C9。产生 1 Hz 的秒脉冲，每秒钟点亮一个 LED。

开始 8 个 LED 都为关闭状态（缺省值为：LEDOut = 8'b0000_0000）；即：

- (0) LEDOut = 8'b0000_0000;
- (1) LED Out = 8'b0000_0001;
- (2) LED Out = 8'b0000_0011;
- (3) LED Out = 8'b0000_0111;
- (4) LED Out = 8'b0000_1111;
- (6) LED Out = 8'b0001_1111;
- (7) LED Out = 8'b0011_1111;
- (8) LED Out = 8'b0111_1111;
- (9) LED Out = 8'b1111_1111;
- (10) 不断重复 (1) ~ (9)

3、模块设计框图

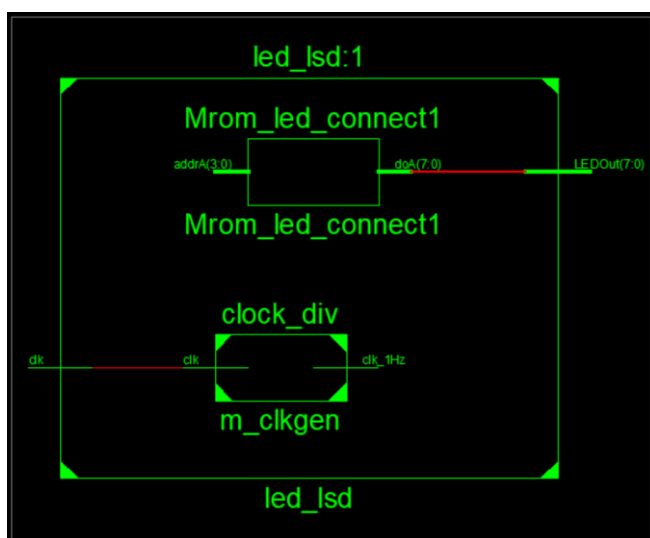 

4、实验原理：

1、LED 原理

Spartan-3e FPGA Starter Kit 板有 8 个独立的表面安装 led 位于滑动开关上方，如图 2-10 所示。led 标记为 LED0 到 LED7。LED7 是最左边的 LED, LED0 是最右边的 LED。

 


Figure 2-10: Eight Discrete LEDs

操作：每个 LED 的一端连接到地，另一端通过 390 欧限流电阻连接到 Spartan-3e 设备上

的引脚。为了点亮单个 LED，需驱动相关的 FPGA 控制信号为高。

UCF 位置约束：图 2-11 提供了四个按钮开关的 UCF 约束，包括 I/O 引脚分配，使用的 I/O 标准，输出回转率和输出驱动电流。

```
NET "LED<7>" LOC = "F9" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LED<6>" LOC = "E9" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LED<5>" LOC = "D11" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LED<4>" LOC = "C11" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LED<3>" LOC = "F11" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LED<2>" LOC = "E11" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LED<1>" LOC = "E12" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LED<0>" LOC = "F12" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
```

Figure 2-11: UCF Constraints for Eight Discrete LEDs

2、50MHz 时钟

如图 3-1 所示，Spartan-3E FPGA Starter Kit 单板支持三个主时钟输入源，它们都位于 Xilinx 标识的下方，靠近 spartan-3e 标识。该板包括一个板载 50 MHz 时钟振荡器。时钟可以通过 SMA 风格的连接器提供。FPGA 也可以通过 SMA 风格的连接器产生时钟信号或其他高速信号。可选安装一个单独的 8 针 DIP 风格时钟振荡器在提供的插座。

 


Figure 3-1: Available Clock Inputs

50MHz 时钟振荡器的 UCF 约束如下图。

```
NET "CLK_50MHZ" LOC = "C9" | IOSTANDARD = LVCMOS33 ;
NET "CLK_SMA" LOC = "A10" | IOSTANDARD = LVCMOS33 ;
NET "CLK_AUX" LOC = "B8" | IOSTANDARD = LVCMOS33 ;
```

Figure 3-2: UCF Location Constraints for Clock Sources

5、Verilog 模块设计

```
// 顶层模块
//led_lsd.v
`timescale 1ns / 1ps
`include "clock_div.v"

module led_lsd(input clk, output [7:0] LEDOut);
```

```

reg [7:0] led_connect;
reg [3:0] state;
wire clk_1;

clock_div m_clkgen(.clk_1Hz(clk_1), .clk(clk));

always @(posedge clk_1) begin
    if (state > 8) state <= 1; //下一个状态就是状态 1, 第一个灯亮
    else state <= state + 1;
end

always@(*)
    case (state)
        1: led_connect<=8'b0000_0001;
        2: led_connect<=8'b0000_0011;
        3: led_connect<=8'b0000_0111;
        4: led_connect<=8'b0000_1111;
        5: led_connect<=8'b0001_1111;
        6: led_connect<=8'b0011_1111;
        7: led_connect<=8'b0111_1111;
        8: led_connect<=8'b1111_1111;
        default: led_connect<=8'b0000_0000;
    endcase
    assign LEDOut = led_connect;
endmodule

// 时钟分频模块
//clock_div.v
module clock_div(output reg clk_1Hz,
    input clk
);

//1Hz 的输出信号需要每 1/2s 翻转一次, 1/2s =25,000,000 个信号脉冲
parameter PULSESCOUNTER = 25'b1_0111_1101_0111_1000_0100_0000, //
25,000,000=1_0111_1101_0111_1000_0100_0000
    RESETZERO = 25'h0;

reg [24:0] counter;

```

```

always @(posedge clk) begin
    if (counter < PULSESCOUNTER)
        counter <= counter + 1'b1;
    else begin
        clk_1Hz <= ~clk_1Hz;
        counter <= RESETZERO;
    end
end
endmodule

```

// ucf 引脚约束

```

NET "clk" LOC = "C9" | IOSTANDARD = LVCMOS33 ;
NET "LEDOut<7>" LOC = "F9" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LEDOut<6>" LOC = "E9" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LEDOut<5>" LOC = "D11" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LEDOut<4>" LOC = "C11" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LEDOut<3>" LOC = "F11" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LEDOut<2>" LOC = "E11" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LEDOut<1>" LOC = "E12" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;
NET "LEDOut<0>" LOC = "F12" | IOSTANDARD = LVTTTL | SLEW = SLOW | DRIVE = 8 ;

```

//测试台模块

```

`include "led_1sd.v"
module tb_led_1sd;
    reg clk;
    wire [7:0]p_led;

    led_1sd    led(.LEDOut(p_led),.clk(clk));

    initial
    begin
        clk=0;
        forever #10 clk=~clk;
    end


    initial
    #3000 $stop;

    initial

```

endmodule

如图，随着 50MHz 时钟信号输入，LED 正确显示流水灯。

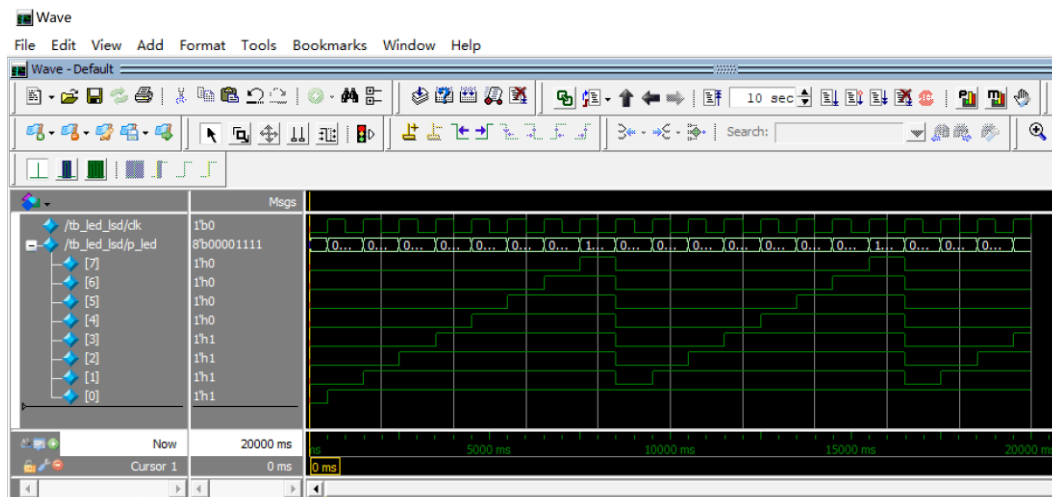

```
VSIM 12> run
# time= 0,ledout=00000000
# time= 5,ledout=00000001
# time= 15,ledout=00000011
# time= 25,ledout=00000111
# time= 35,ledout=00001111
# time= 45,ledout=00011111
# time= 55,ledout=00111111
# time= 65,ledout=01111111
# time= 75,ledout=11111111
# time= 85,ledout=00000001
# time= 95,ledout=00000011
VSIM 13> run
# time= 105,ledout=00000111
# time= 115,ledout=00001111
# time= 125,ledout=00011111
# time= 135,ledout=00111111
# time= 145,ledout=01111111
# time= 155,ledout=11111111
# time= 165,ledout=00000001
# time= 175,ledout=00000011
# time= 185,ledout=00000111
# time= 195,ledout=00001111
```